

<b>Chapter One.....</b>	11
Introduction .....	11
What You Will Learn.....	12
Who Will Benefit from This Book? .....	13
The General Format of This Book .....	13
Why Measure? .....	14
Obtain or Validate Data .....	14
Design, Selection and Optimization .....	17
Troubleshooting .....	18
Validation or Verification .....	20
Terminology.....	21
Measurement .....	21
High Fidelity .....	21
Precise.....	22
Non-Invasive .....	22
Indirect Measurement .....	23
In-Situ or In-Circuit .....	23
<b>Chapter Two .....</b>	24
Measurement Philosophy .....	24
Cause No Damage.....	24
Measure without Influencing the Measurement.....	25
Validate the Test Setup and Measurement Limits .....	27
Measure in the Most Efficient and Direct Way .....	28
Non-Invasive vs. Invasive Measurement .....	28
In-Situ Measurement .....	29
Indirect vs. Direct Measurement.....	29
Document Measurements Thoroughly .....	30
The Test Engineer and Contact Information .....	31
The Purpose of the Test.....	31
Simulated or Expected Results If Available .....	33
The Date and Physical Location of the Testing.....	34
Operational Test Environment and Conditions.....	35
The Model of Each Piece of Test Equipment (Including Probes) and Verification they are Calibrated.....	36
Setup Diagram and/or Photograph .....	36
Measurement Annotations and Comments .....	38

Any Observed Anomalies .....	38
Summary of the Results and any Follow-On Work .....	38
<b>Chapter Three.....</b>	<b>39</b>
Measurement Fundamentals .....	39
Sensitivity .....	39
Noise Floor .....	41
Dynamic Range .....	43
Noise Density .....	49
Signal Averaging .....	54
Scaling .....	57
Attenuators .....	59
Preamplifiers .....	60
Linear vs. Log display .....	62
Measurement Domains .....	64
Frequency Domain .....	64
Gain and Phase .....	65
S-Parameters .....	66
Impedance .....	67
Time Domain .....	68
Spectrum Domain .....	71
Comparing Domains .....	74
Tips and Tricks.....	76
Chapter References .....	77
<b>Chapter Four .....</b>	<b>78</b>
Test Instruments .....	78
Frequency Response Analyzers and Vector Network Analyzers .....	80
The OMICRON Lab Bode 100—Key Features .....	81
Agilent Technologies E5061B—Key Features .....	82
Oscilloscopes .....	83
Teledyne Lecroy Waverunner 640Zi—Key Features ....	84
Rohde & Schwarz RTO1044—Key Features .....	85
Tektronix DPO7354C—Key Features.....	86

## Power Integrity

Tektronix DPO72004B Key Features .....	87
Waverunner 845Zi—Key Features .....	88
Tektronix MSO5204—Key Features.....	89
Teledyne Lecroy HDO6104—Key Features.....	90
Tektronix MDO4104-6—Key Features .....	91
OMICRON Lab ISAQ 100—Key Features .....	92
Spectrum Analyzers .....	93
Tektronix RSA5106—Key Features.....	93
Agilent Technologies N9020A—Key Features .....	94
Agilent Technologies E5052B—Key Features .....	95
Signal Generators.....	96
Agilent Technologies E8257D—Key Features .....	96
TDR/TDT S-Parameter Analyzers.....	97
PICOTEST G5100A—Key Features .....	97
TDR/TDT.....	98
Tektronix DSA8300—Key Features .....	98
Tektronix 80E10—Key Features .....	99
Teledyne Lecroy SPARQ 4012E—Key Features .....	100
Agilent Technologies E5071C Key Features .....	101
<b>Chapter Five.....</b>	<b>102</b>
Probes, Injectors and Interconnects .....	102
Voltage Probes .....	102
Probe Circuit Interaction .....	105
Flattening the Probe Response .....	109
Confirming Measurements .....	111
Selecting a Voltage Probe .....	113
Passive Probes.....	114
Active Probes .....	116
Key Features for ZS2500 (ZS4000).....	117
Differential Probes .....	117
Specialty Probes .....	118
Low Impedance Probes .....	118
Multiport Probes .....	119
Port Splitter .....	119

Performance Probes .....	121
Direct Coaxial Cables.....	122
Current Probes.....	123
Insertion Impedance.....	125
Improving Sensitivity .....	127
Differential or Common Mode Current .....	127
Near-Field Probes .....	128
Signal Injectors.....	129
Injection Transformers .....	130
Solid State Voltage Injectors.....	131
Solid-State Current Injectors .....	132
Specialty Coaxial Cables.....	132
DC Bias/Blocker.....	132
Attenuators .....	133
Line Injector .....	133
Preamplifier .....	133
Common Mode Transformers .....	134
Impedance Fixtures .....	134
Other Connections .....	135
Banana Leads .....	135
Chapter References .....	136
<b>Chapter 6.....</b>	<b>137</b>
The Distributed System .....	137
Noise Paths within a Voltage Regulator .....	138
Internal Noise .....	140
Power Supply Rejection Ratio (PSRR) .....	143
Output Impedance .....	145
Reverse Transfer and Crosstalk .....	146
Control Loop Stability .....	148
Impact on Output Impedance .....	149
Impact on Noise.....	150
Impact on PSRR .....	152
Impact on Reverse Transfer .....	152
How Poor Stability Propagates Through the System.....	154

## Power Integrity

Adding the PDNs .....	157
Chapter References .....	160
<b>Chapter 7 .....</b>	<b>161</b>
Measuring Impedance.....	161
Selecting a Measurement Method .....	161
Single Port Measurements .....	162
Introduction.....	162
Pros .....	163
Cons .....	164
Tips and Tricks .....	164
Device Setup .....	165
Calibrating the Single Port Measurement.....	167
DC Coupled vs AC Coupled .....	169
Examples.....	169
Two Port Measurements.....	183
Introduction.....	183
Pros .....	190
Cons .....	190
Tips and Tricks .....	191
Device Setup .....	192
Calibrating the Two Port Measurement .....	193
AC-Coupled, Two-Port Shunt-Thru Measurement.....	193
Connecting to the DUT .....	194
Examples.....	196
Current Injection Measurements .....	209
Pros .....	211
Cons .....	211
Solid State .....	211
Transformer Coupled .....	211
Tips and Tricks .....	212
Device Setup .....	212
Examples.....	213
Impedance Adapters .....	215
Pro .....	215

Cons .....	216
Tips and Tricks .....	216
Device setup.....	216
Calibrating the Impedance Adapters .....	217
Examples.....	219
Chapter References .....	223
 <b>Chapter 8.....</b>	 225
Measuring Stability .....	225
Stability and Why it Matters.....	225
Control Loop Basics.....	226
Gain Margin, Phase Margin, Delay margin and Stability Margin .....	229
Bode Plots and Nyquist Charts .....	230
Open Loop Measurement.....	237
Selecting an Injection Point.....	239
Measuring High Voltage Loops .....	241
Injection Devices .....	242
Transformers.....	242
Injection Resistor.....	242
Solid State Injectors .....	244
Probes .....	245
Calibrating the Setup .....	245
Small Signal vs. Large Signal .....	246
Example.....	247
Tips and Tricks .....	252
Closed Loop Measurement .....	253
On and Off Measurements .....	253
Forward Measurements .....	255
Minor Loop Gain .....	256
Non-Invasive Closed Loop Measurement .....	261
Examples.....	262
Tips and Tricks .....	268
Chapter References .....	269

# Power Integrity

<b>Chapter 9 .....</b>	270
Measuring PSRR .....	270
Measurement Methods .....	271
In-Circuit or Out-of-Circuit .....	272
Direct or Indirect Measurement.....	272
Modulating the Input .....	273
Line Injector.....	275
Current Injector .....	280
DC Amplifier.....	282
Choosing the Measurement Domain .....	282
VNA .....	283
Spectrum Analyzer .....	283
Oscilloscope .....	284
Probes and Sensitivity.....	284
Tips and Tricks.....	289
Examples .....	290
Chapter References .....	300
<b>Chapter 10 .....</b>	301
Reverse Transfer and Crosstalk .....	301
Reverse Transfer of Various Topologies .....	303
Series Linear Regulators .....	303
Shunt Regulators .....	304
POL Regulators .....	305
Operational Amplifiers.....	305
Modulating the Output Current.....	306
Current Injector .....	306
DC Bias Injector .....	307
Measuring the Input Current.....	307
Calibrating the Measurement .....	308
VRTS01 Input Current Port .....	308
Current Probe.....	310
Measuring the Input Voltage .....	312
Calibrating the Measurement .....	313
Indirect Measurement .....	315

Tips and Tricks .....	315
Examples.....	315
Chapter References .....	323
<b>Chapter 11 .....</b>	<b>324</b>
Measuring Step Load Response .....	324
Generating the Transient .....	325
Current Injector vs. Electronic Load .....	325
Slew Rate .....	327
Current Modulation Waveform .....	330
Measuring the Response(s).....	333
Large Signal vs. Small Signal .....	333
Notes about Averaging .....	334
Sample Rate and Time Scale.....	337
Additional Examples .....	338
Tips and Tricks .....	345
Chapter References .....	347
<b>Chapter 12 .....</b>	<b>348</b>
Measuring Ripple and Noise .....	348
Selecting a Measurement Method .....	349
In or Out of System .....	349
Direct or Indirect.....	350
Time or Spectral Domain .....	350
Connecting the Equipment .....	351
Passive Scope Probes .....	351
Pros .....	351
Cons .....	352
Tips and Tricks .....	352
Active Scope Probes.....	352
Pros .....	352
Cons .....	353
Tips and Tricks .....	353
Direct 50Ω Terminated Connection .....	353
Pros .....	353

## Power Integrity

Cons .....	353
Tips and Tricks .....	354
Choosing the Equipment .....	354
Examples .....	356
Spectral Domain Examples .....	356
Time Domain Examples.....	364
Indirect Measurement Examples .....	369
In-Circuit Examples.....	374
Averaging and Filtering.....	376
Chapter References .....	377
 <b>Chapter 13 .....</b>	 378
Measuring Edges .....	378
Relating Bandwidth and Rise Time.....	379
Cascading Rise Times .....	384
Impact of Filters and Bandwidth Limiting.....	388
Sampling Rate and Interleaved Sampling.....	392
Interpolation.....	394
Coaxial Cables .....	395
Effects of High Frequency Losses.....	396
Velocity Factor and Timing Delay .....	397
The Criticality of the Probe Connection .....	398
Printed Circuit Board Issues .....	403
Probes .....	403
Example 1: Measuring an Edge with Active and Passive Probes .....	404
Example 2: Rise Time of a High-Voltage Probe .....	406
Tips and Tricks .....	408
Chapter References .....	409
 <b>Chapter 14 .....</b>	 410
Troubleshooting with Near Field Probes.....	410
The Basics of Emissions.....	411
Near Field Probes .....	414
Probe and Orientation.....	415

Steven M. Sandler

The Measurement Instrument .....	419
Spectrum Gating .....	420
Examples .....	422
Tips and Tricks .....	439
Chapter References .....	440
<b>Chapter 15 .....</b>	<b>441</b>
Higher Frequency Impedance Measurements .....	441
Time Domain.....	442
TDR.....	443
Calibration .....	444
Reference Plane.....	445
Setting TDR Pulse Rise Time .....	451
Interpreting TDR Measurements .....	452
Estimating Inductance and Capacitance.....	458
Tips and Tricks .....	466
S-parameter Measurements .....	466
Chapter References .....	470
<b>Afterword by Robert Bolanos—Power Integrity in a Changing Landscape .....</b>	<b>471</b>